



Electrical Engineering Department  
**University of Engineering & Technology**  
Peshawar, Mardan Campus

**Circuit Analysis - II**

**Assignment # 4(b)**

**Due date: 1<sup>st</sup> May**

- 1. Exercise Questions 13.50 (b & c)**
- 2. Exercise Questions 13.54, 13.55 & 13.59**
- 3. Exercise Questions 13PFE-5 (a) [2<sup>nd</sup> order derivative]**

From: Basic Engineering Circuit Analysis – Ed-10; J. David Irwin