
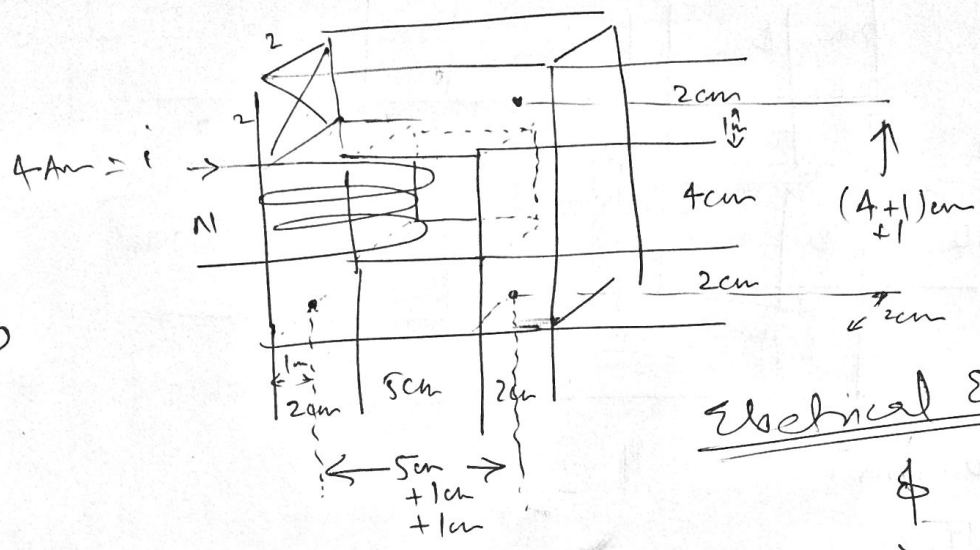


1

$\Phi = ?$
 $\mu = 1500$
 $N = 50$

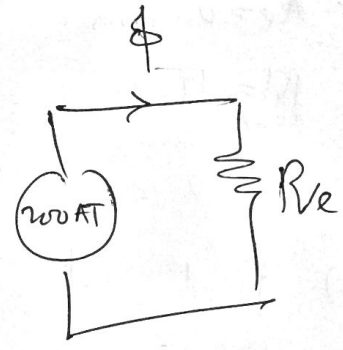

Electrical Equivalent



Total length = $7\text{cm} + 7\text{cm} + 6\text{cm} + 6\text{cm}$
 $l_e = 26\text{cm} = 26 \times 10^{-2}\text{m}$
 effective area = $0.02 \times 0.02 = 4 \times 10^{-4}\text{m}^2$

$$R_e = \frac{l_e}{\mu_0 \mu_r A_e}$$

$$R_e = \frac{1}{1500 \times 4\pi \times 10^{-7}} \times \frac{26 \times 10^{-2}}{4 \times 10^{-4}}$$

$$= 0.000344 \times 10^{-2+4+7} \text{ AT/Wb}$$


$$R_e = 344 \times 10^3 \text{ AT/Wb}$$

$$\Phi = \frac{Ni}{R_e}$$

$$= \frac{4 \text{ ampere} \times 50 \text{ turns}}{344 \times 10^3 \text{ AT/Wb}}$$

$$\Phi = 0.58 \times 10^{-3} \text{ Wb}$$


2)

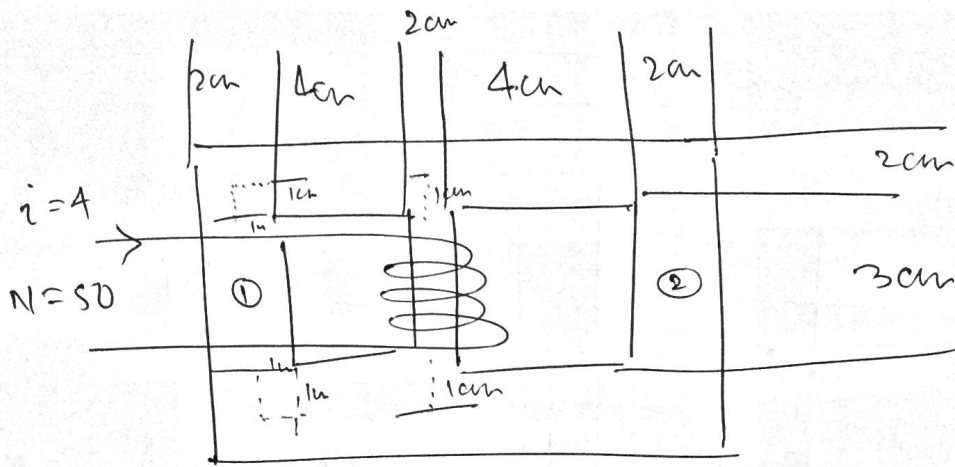

$$A_e = 0.25 \text{ m}^2$$

$$\mu = 1700$$

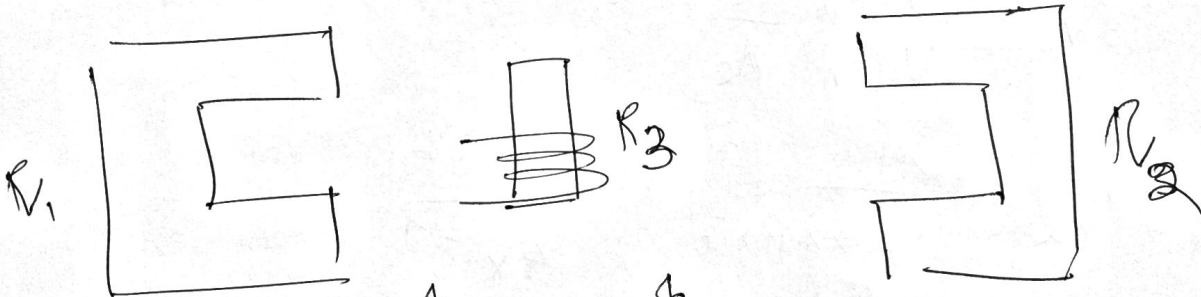- a) Draw equivalent circuit in electrical components.
 - b) Find Φ in arm 2
- find Magnetization intensity H in arm 2



$$l_{e1} = 1\text{cm} + 4\text{cm} + 1\text{cm} + 3\text{cm} + 1\text{cm} + 1\text{cm} + 4\text{cm} + 1\text{cm}$$


$$= 16\text{cm} = l_{e2}$$

$$l_{e3} = 3\text{cm} + 1\text{cm} + 1\text{cm} = 5\text{cm}$$

$$R_1 = \frac{1}{\mu_0 \mu_r} \frac{l e_1}{A_e} = x \quad (3)$$

$$R_2 = \frac{1}{\mu_0 \mu_r} \frac{l e_2}{A_e} = y$$
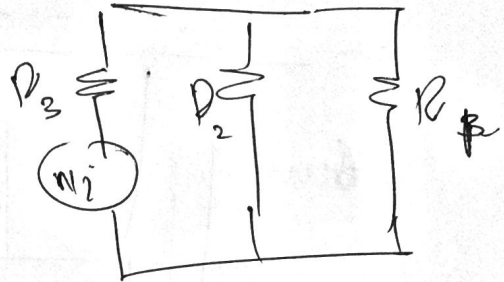
$$R_3 = \frac{1}{\mu_0 \mu_r} \frac{l e_3}{A_e} = z$$



$$R_{total} = R_3 + R_1 // R_2$$

$$= z + \frac{xy}{x+y}$$

$$R_{total} = w \quad (A/m)$$

$$\phi_{total} = \frac{Ni}{R_{total}} = \frac{200}{w}$$

$$\phi_2 = \phi_{total} * \frac{R_1}{R_1 + R_2} \quad \left. \vphantom{\phi_2} \right\} \text{current divider rule}$$


$$\phi_2 = \psi \quad (wb)$$

$$\phi_2 = B_2 A_2$$

$$\phi_2 = \mu_0 \mu_r H_2 A_2 \quad \because A_2 = A_e$$

$$H_2 = \frac{\phi_2}{\mu_0 \mu_r A_e} \quad (A/m)$$

find R of magnetic circuit gm

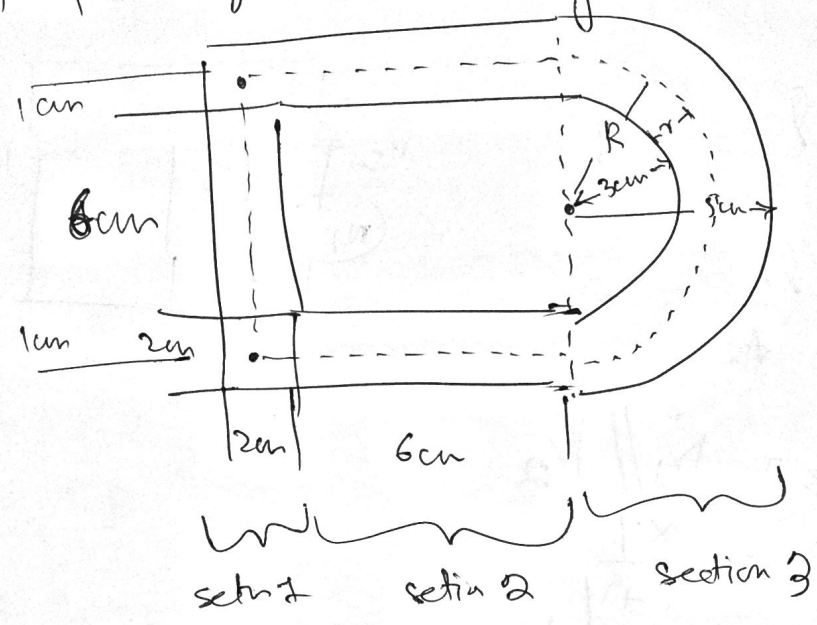

$$A_e = 0.25 \text{ m}^2$$

$$\mu_r = 1600$$

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

$$A_{e1} = 0.25 \text{ m}^2$$

$$l_{e1} = 1\text{cm} + 6\text{cm} + 1\text{cm} = 8\text{cm} = 8 \times 10^{-2} \text{ m}$$

$$R_1 = \frac{1}{1600 \times 4\pi \times 10^{-7} \left(\frac{\text{H}}{\text{m}}\right)} \times \frac{8 \times 10^{-2} \text{ m}^2}{0.25 \text{ m}^2} = x \text{ (AT/Wb)}$$

$$A_{e2} = 0.25 \text{ m}^2$$

$$l_{e2} = (1\text{cm} + 6\text{cm}) \times 2 = 14\text{cm} = 14 \times 10^{-2} \text{ m}$$

$$R_2 = \frac{1}{1600 \times 4\pi \times 10^{-7}} \times \frac{14 \times 10^{-2}}{0.25 \text{ m}^2} = y \text{ (AT/Wb)}$$

$$A_{e3} = 0.25 \text{ m}^2$$

$$r = \frac{5\text{cm} - 3\text{cm}}{2} = \frac{2\text{cm}}{2} = 1\text{cm}$$

$$R = 3\text{cm} + 1\text{cm} = 4\text{cm}$$

$$l_{e3} = \frac{2\pi R}{2} = \pi(R) : \text{Half circle} = 12.56\text{cm} = 12.56 \times 10^{-2} \text{ m}$$

$$R_3 = \frac{1}{1600 \times 4\pi \times 10^{-7}} \times \frac{12.56 \times 10^{-2}}{0.25 \text{ m}^2} = z \text{ (AT/Wb)}$$

$$R = R_1 + R_2 + R_3$$

Transformer

3

①

$$V_{in} = 200 \text{ V}$$

$$V_{out} = 400 \text{ V}$$

$$I_{in} = 300 \text{ A}$$

$$I_{out} = ?$$

$$\frac{N_1}{N_2} = ?$$

$$V_1 I_1 = V_2 I_2$$

$$200 \times 300 = 400 \times I_2$$

$$\frac{200}{2} = I_2$$

$$I_2 = 150 \text{ A}$$

$$\frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{V_i}{V_o} = \frac{200}{400} = \frac{1}{2}$$

$$\frac{N_1}{N_2} = \frac{1}{2}$$

②


find efficiency of transformer for $V_{out} = V_{in}$
and $I_{out} = 0.99 I_{in}$

$$\eta = \frac{\text{output power}}{\text{input power}} = \frac{0.99 I_{in} \times V_{in}}{I_{in} V_{in}}$$

$$\eta = 0.99$$

$$\eta\% = 99\%$$

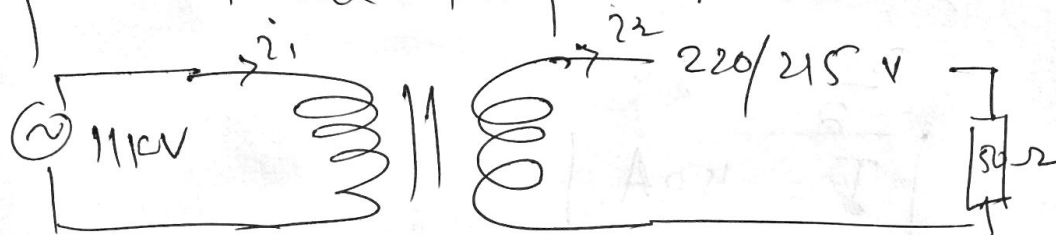③ A load of $50\ \Omega$ is connected to a transformer due to which the voltage is reduced from no load voltage of 220V at the output to 215V at the output for a constant input voltage 11000 volts . Find the voltage regulation and the power taken by the load as well as the loss of power inside transformer.



Soln

$$\% \text{ regulation} = \frac{V_{\text{no-load}} - V_{\text{full-load}}}{V_{\text{full-load}}} \times 100\%$$

$$= \frac{220\text{V} - 215\text{V}}{215\text{V}} = \frac{500}{215} \%$$

$$\% \text{ Reg} = 2.32\%$$

$$I_{\text{ent}} = \frac{215\text{V}}{50\ \Omega} = 4.3\text{ A}$$

$$I_{\text{ent no loss}} = \frac{220\text{V}}{50\ \Omega} = 4.4\text{ A}$$

$$\Delta I_{\text{ent}} = 0.1\text{ A}$$

$$\text{Turn ratio} = \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{11K}{220} = 50$$

(6)

$$V_{in} \text{ for } 25V = 25 \times 50 = 10750 \text{ Volts}$$

$$\Delta V_{in} = 11000 - 10750 = +250 \text{ V}$$

$$\Delta I_{in} = \frac{0.1}{50} = 0.002 \text{ A}$$

$$P_{loss, in} = \Delta V_{in} \times \Delta I_{in} \\ = 0.002 \times 250$$

$$P_{in, loss} = 0.5 \text{ watt} \quad \checkmark$$

$$P_{out} = \Delta V_{out} \Delta I_{out} \\ = 5 \times 0.1 \\ P_{out} = 0.5 \text{ watt} \quad \checkmark$$

$$\text{Total } I_{in} = \Delta I_{in} + I_{in}$$

$$\text{Total } P_{in} = P_{out} + P_{loss} = P_{out, loss}$$

$$= \cancel{4.3} (4.3)^2 \times 50 + (0.1)^2 \times 50$$

$$= (4.3 + 0.1)^2 \times 50$$

$$= (4.4)^2 \times 50 = I_{total}^2 \times R$$


$$P_{total} = 968 \text{ watt}$$

$$\eta = \frac{P_{out}}{P_{in, total}} = \frac{968 - 0.5}{968}$$

$$\eta = 0.99948$$


$$\eta \% = 99.948\%$$

Flux division in parallel

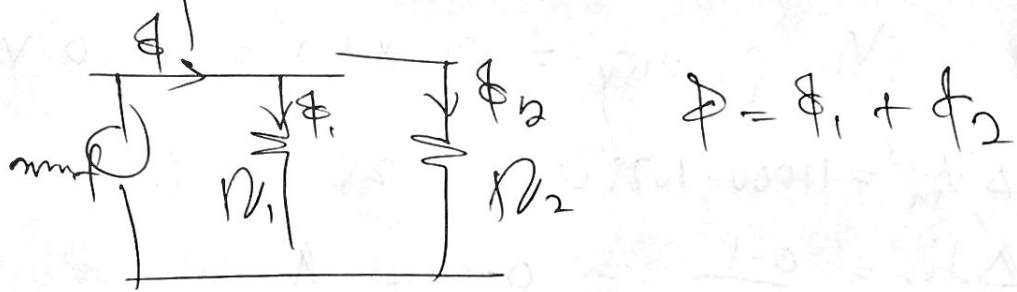

$$\phi_{(2)} = \phi \times \frac{R_{(1)}}{R_1 + R_2}, \quad \phi_{(1)} = \phi \times \frac{R_{(2)}}{R_1 + R_2}$$

mmf division in series.

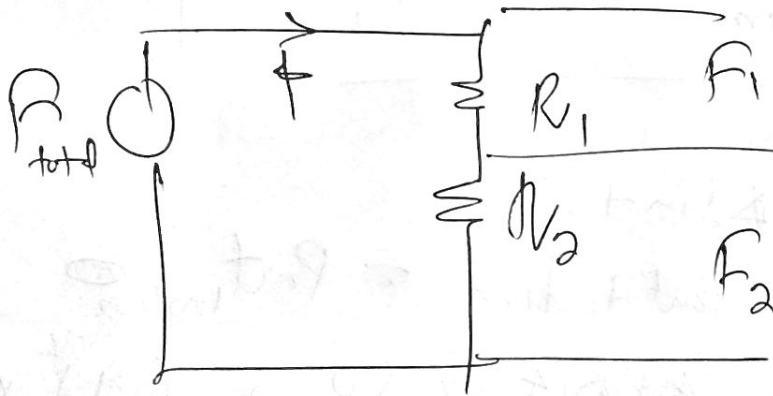

$$F_2 = \phi R_2, \quad F_1 = \phi R_1$$

$$F_{(2)} = F_{total} \times \frac{R_{(2)}}{R_1 + R_2}, \quad F_1 = F_1 + F_2$$

$$F_{(1)} = F_{total} \times \frac{R_{(1)}}{R_1 + R_2}$$