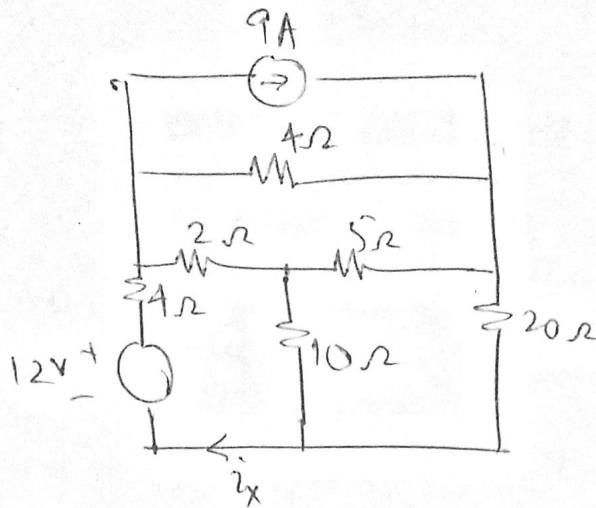


Example
2-5




(1)

Find $V_{5\Omega}$ and i_x
using KCL

Solution

KCL = sum of current on a junction equals zero
 \rightarrow entry \leftarrow leaving

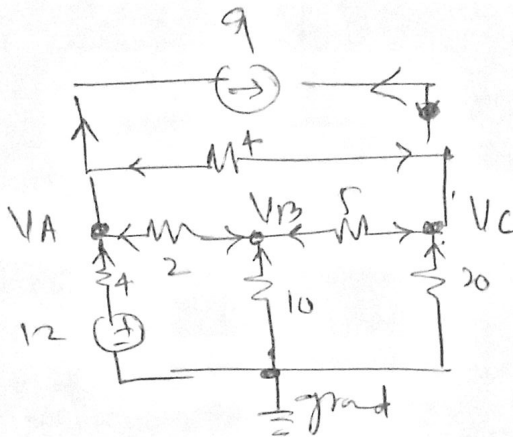Mark all junctions and consider one as zero potential ground.



$$\sum \text{entry } I = \sum \text{leaving } I$$

at VA (all current toward A are $V_A - V_x$)

Current leaving.

$$\frac{V_A - 0 - 12}{4} + \frac{V_A - V_B}{2} + \frac{V_A - V_C}{4} + 9 = 0$$

$$V_A \left(\frac{1}{4} + \frac{1}{2} + \frac{1}{4} \right) + V_B \left(\frac{1}{2} \right) - V_C \left(\frac{1}{4} \right) = 3 - 9 = -6$$

$$V_A (1) - 0.5 (V_B) - 0.25 V_C = -6 \quad \text{--- (1)}$$

at V_B

$$\frac{V_B - V_A}{2} + \frac{V_B - 0}{10} + \frac{V_B - V_C}{5} = 0$$

$$-0.5 V_A + 0.8 V_B - 0.2 V_C = 0 \quad \text{--- (2)}$$

Current leaving

$$\frac{V_C - 0}{20} + \frac{V_C - V_B}{5} + \frac{V_C - V_A}{4} - 9 = 0$$

$$-0.25 V_A - 0.25 V_B + 0.3 V_C = 9 \quad \text{--- (3)}$$

2


$V_A = 4$ $V_B = 8.33V$ $V_C = 23.3V$

$$V_{5\Omega} = V_B - V_C$$
$$\boxed{V_{5\Omega} = -15V}$$

$$-i_x = \frac{V_A - 0 - 12}{4}$$

$$-i_x = 4 \frac{-12}{4} = \frac{-8}{4} = -2A$$

$$\boxed{i_x = 2A}$$

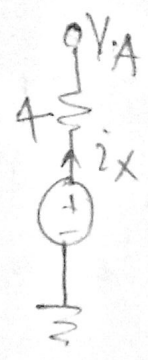

08

$$0 - V_A + 12 = i_x \cdot 4$$
$$\frac{-4 + 12}{4} = i_x$$
$$\boxed{i_x = 2}$$