

$$z_{11} = 3\Omega$$

$$z_{12} = 5\Omega$$

$$z_{21} = 6\Omega$$

$$z_{22} = 10\Omega$$

$$z_L = 10\Omega$$

Z-parameters given

(1)

find I_L for $V_1 = 30V$


solution

equations

$$V_1 = I_1 z_{11} + I_2 z_{12} \quad \text{--- (1)}$$

$$V_2 = I_1 z_{21} + I_2 z_{22} \quad \text{--- (2)}$$

Diagram

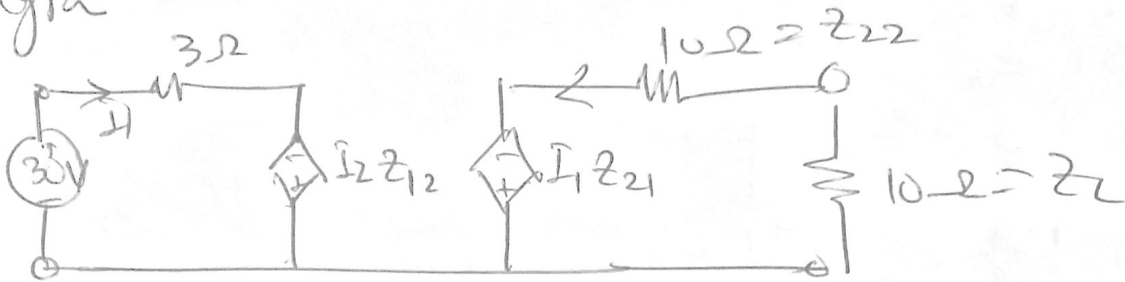

new equations

$$\text{(1)} \Rightarrow 30V = I_1(3) + I_2(5)$$

$$0 = I_1(6) + I_2(10 + 10)$$

Solve for I_1 and I_2

$$I_L = I_2 = \text{answer.}$$

Note: we can clearly see that once we find the $[Z]$ matrix we easily add z_{22} and z_L to solve the problem.

▶ The same method will add V_{22} with V_L is parallel

$$Y_{11} = 0.5$$

$$Y_{12} = 0.2$$

$$Y_{21} = 1$$

$$Y_{22} = 0.333$$

Y-parameters gives

(2)

If a Load $Y_L = 0.2 \Omega$ is connected at output
find I_L (out current) ? for $V_1 = 5$ volts



$$I_1 = V_1 Y_{11} + V_2 Y_{12}$$

$$I_2 = V_1 Y_{21} + V_2 Y_{22}$$



$$Y_L = \frac{1}{Z_L} = 0.2$$
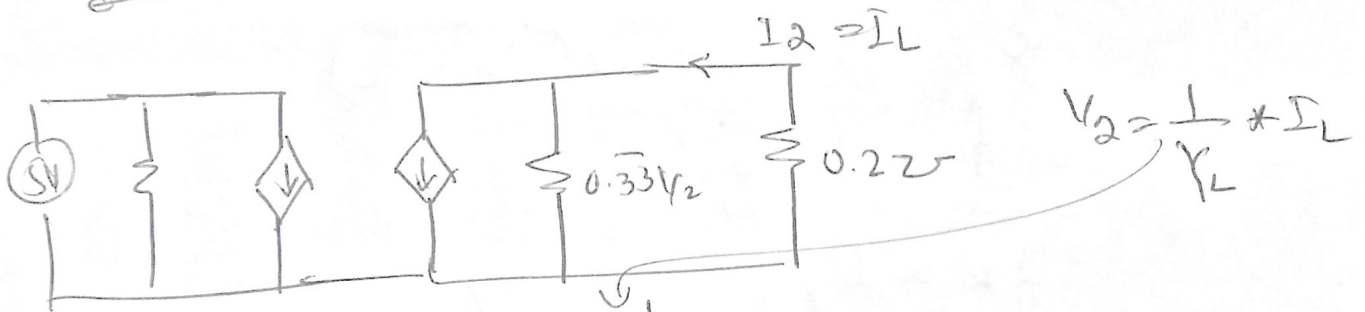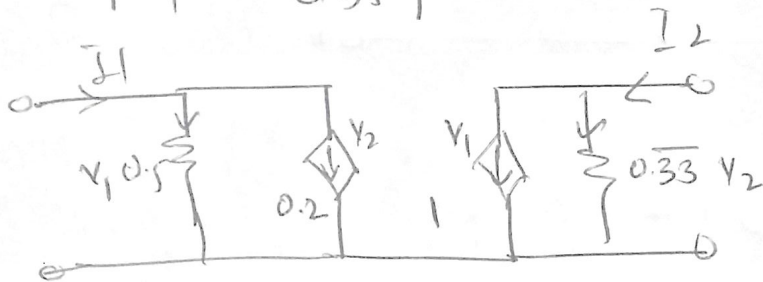
$$[Y] = \begin{bmatrix} 0.5 & 0.2 \\ 1 & 0.333 \end{bmatrix}$$




$$\textcircled{1} \Rightarrow I_1 = 5(0.5) + (I_2 * \frac{1}{0.2})(0.2)$$


$$\textcircled{2} \Rightarrow I_2 = 5(1) + (I_2 * \frac{1}{0.2})(0.2 + 0.333)$$

Solve for I_1 and I_2

Ex 16.1

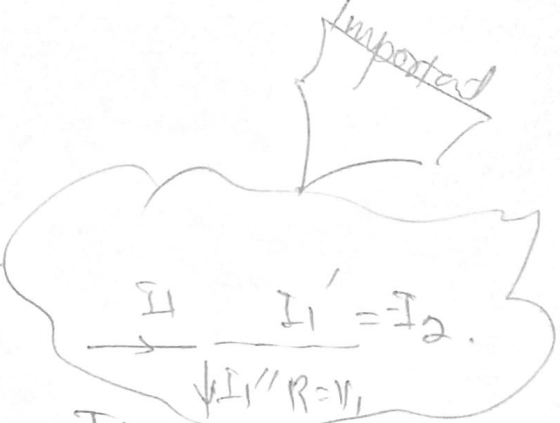

$V_2 = 0$

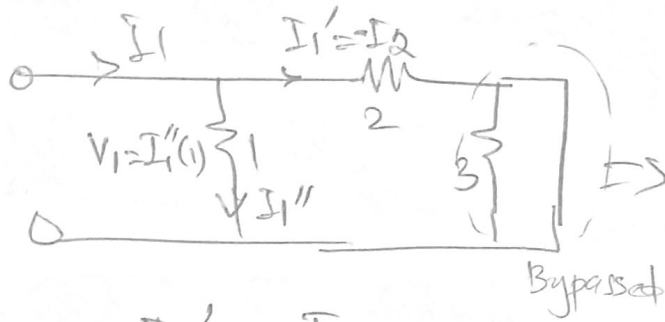

Finding Current in each branch

$$I_1' = -I_2$$


$$I_1' = I_1 \left(\frac{1}{3} \right) \quad I_1'' = I_1 \left(\frac{2}{3} \right)$$

$$-I_2 = \frac{I_1}{3}$$

$$Y_{11} = \frac{I_1}{V_1} = \frac{I_1}{I_1''(1\Omega)} = \frac{I_1}{I_1 \left(\frac{2}{3} \right) 1} = \frac{3}{2} S$$

$$Y_{21} = \frac{I_2}{V_1} = \frac{-I_1'}{I_1''(1\Omega)} = \frac{-\frac{I_1}{3}}{\frac{2}{3} I_1 (1)} = -\frac{1}{2} S$$

$V_1 = 0$

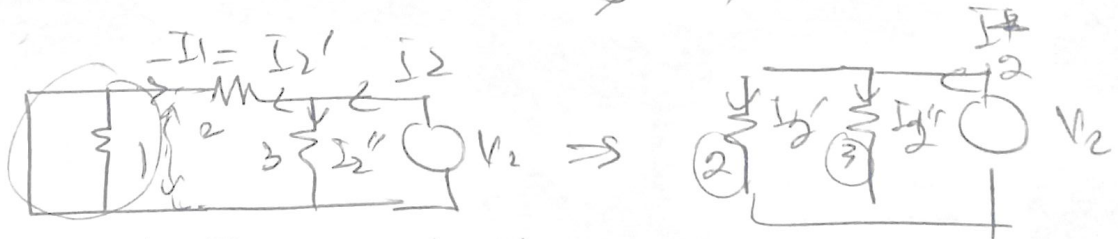

Finding Current in each branch

$$I_2' = -I_1 = I_2 \left(\frac{3}{5} \right)$$

$$I_2'' = I_2 \left(\frac{2}{5} \right)$$

$$Y_{12} = \frac{I_1}{V_2} = \frac{-I_2 \left(\frac{3}{5} \right)}{I_2''(3)} = \frac{-\frac{I_2}{5}}{\frac{2}{5} I_2 (3)} = -\frac{1}{2} S$$

$$Y_{22} = \frac{I_2}{V_2} = \frac{I_2}{I_2''(3)} = \frac{I_2}{\frac{2}{5} I_2 (3)} = \frac{5}{6} S$$