

Q: No. 1: Encircle the best possible answer.

(10)

- i) We use ____ types of combination while dealing with star and delta w.r.t per phase impedance.
- 1
 - 2
 - 3
 - Can't be determined
- ii) Line voltage is greater than phase voltage in ____.
- Star combination
 - Wye combination
 - Delta combination
 - Both (a) and (b)
- iii) Semi-Logarithmic graph is used for ____.
- Converting non-linear function to linear
 - Converting addition to multiplication
 - Representing decimal number as a whole number
 - All of the above
 - Only (b) and (c)
- iv) Quality factor is the reciprocal of ____.
- Diversity Factor
 - Power Factor
 - Line impedance
 - None of the above
- v) Transfer function gives us an insight of the system w.r.t ____.
- Input Signal
 - Only Frequency of Input signal
 - Structural components of the system
 - Only (a) and (c)
 - Only (b) and (c)
- vi) In Parallel RLC circuit. The offered impedance of the circuit is ____ at the resonance frequency.
- Maximum
 - Minimum
 - Same as at non-resonating condition
- vii) A signal is centered at **700Hz** with a deviation of 100Hz. What should be the tuning frequency f_c (rad/s) of Series RLC circuit to pass the signal?
- $2\pi \cdot 700$ rad/s
 - $2\pi \cdot 600$ rad/s
 - $2\pi \cdot 800$ rad/s
 - $2\pi \cdot 200$ rad/s
 - 600 rad/s
- viii) System pole(s) determines the range of frequency where the input signal will be ____.
- Enhanced
 - Degraded
 - Doesn't affect
- ix) Negative sign with logarithm quantity indicates ____.
- Attenuation
 - Gain
 - Noise
 - None of the above
- x) The phase angle of a system having pole at $j\omega=5$ and a zero at $j\omega=15$ will reside between
- 90° and 0°
 - -90° and 0°
 - 90° and -90°
 - Always at 0°

Q: No. 2:

(6)

- What is the main difference between positive sequence and negative sequence current in 3 phase power system?
- What are the benefits of 3 phase delta over 3 phase star transmission lines?
- One phase of wye connected load is short-circuited with the help of a wire having 0Ω resistance. How can we suppose that it resembles to an open delta configuration?

Q: No. 3: A star configured load is connected through a 3 phase transmission line with a **120V rms** delta connected positive sequenced source configuration having $\theta_{ab} = 0^\circ$? Considering

load's per phase impedance of $Z_L = 2 + j3 \Omega$ and line impedance of 0Ω , determine the phase voltages, currents and per phase total power (S) for the connected load. (4)

Q: No. 4: For the circuit in **Fig. 1**, find the voltage gain ($A_v(s)$) and current gain ($A_i(s)$) in terms of complex frequency $s = j\omega$. (10)

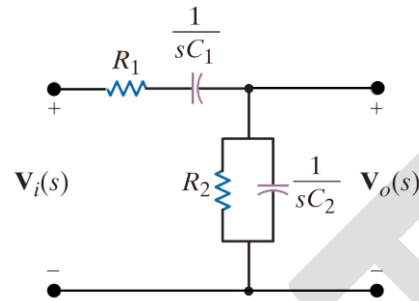


Fig. 1

Hint: Voltage and current dividend rules can find the ratios

Q: No. 5: (20)

The half power bandwidth of a series RLC circuit is **2kHz**. If the circuit is to be designed from an inductive component of 0.1mH and a capacitive component of $5\mu\text{F}$:

- i) What will be the central tuning frequency (f_c) of the circuit?
- ii) What will be the lower bound (f_L) and upper bound (f_H) of the Bandwidth?
- iii) Determine the quality factor of the filter for **$R=20\Omega$, 30Ω and 100Ω** .
- iv) Is the designed circuit useful in filtering out a voltage signal of **6.5kHz** from a noise band of **20Hz-20kHz**?
- v) Draw the frequency vs gain plot for the designed filter.