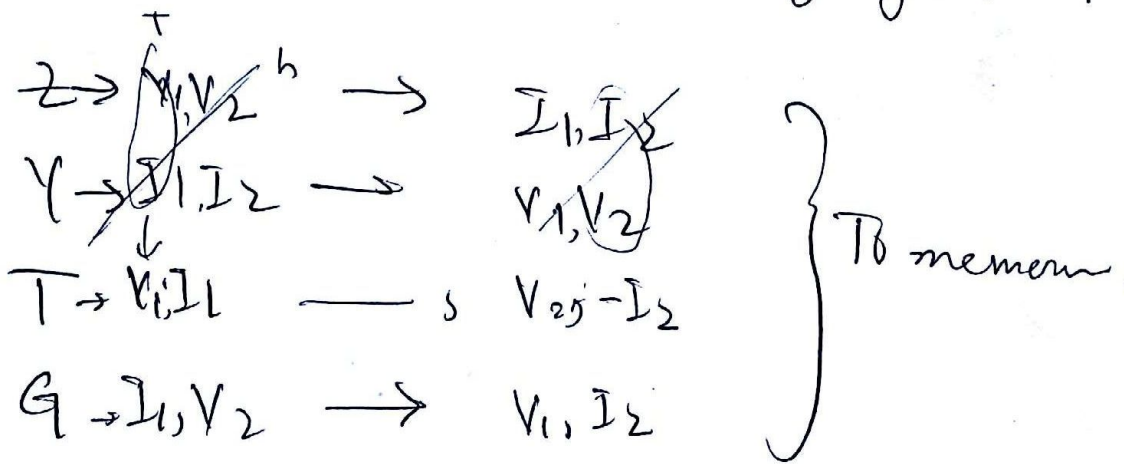


# Two port Network

(1)

- Regarded as black box
- one input / one output port
- $I_{in} = -I_{out}$  but not always.
- Transmission lines, small signal models, i/f. filters are example.
- Described by  $2 \times 2$  matrix
- $Z, Y, \text{ and } ABCD$  parameters are used  
Transmission
- Super position, closed and open tests are used to solve for variables.
- Energy, power, frequency parameters are linked by ports.
- Reciprocal network: having all passive elements
- Symmetrical network: in and out are dual of one another

Parameter	we express	In terms of	Matrix
$\checkmark Z$	$V_1, V_2$	$I_1, I_2$	$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$
$\checkmark Y \neq \frac{1}{Z}$	$I_1, I_2$	$V_1, V_2$	$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$
$\checkmark T$	$V_1, I_1$	$V_2, -I_2$	$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$
<del>H</del>	$V_1, I_2$	$I_1, V_2$	$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$
$\checkmark G$	$I_1, V_2$	$V_1, I_2$	$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$



impedance parameters

2)

$$[V] = [Z] [I]$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$I_1 = 0$$

$$V_1 = Z_{12} I_2 \Rightarrow Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$I_2 = 0$$

$$V_2 = Z_{22} I_2 \Rightarrow Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

$$I_2 = 0$$


$$\begin{aligned} V_1 &= Z_{11} I_1 \\ Z_{11} &= \frac{V_1}{I_1} \Big|_{I_2=0} \\ \text{also } Z_{21} &= \frac{V_2}{I_1} \Big|_{I_2=0} \end{aligned}$$

$Z_{12}$  = reverse transfer function (in 1 due to 2)


$Z_{22}$  = output driving function

$Z_{11}$  = input driving function

$Z_{21}$  = forward T/F (in 2 due to 1)

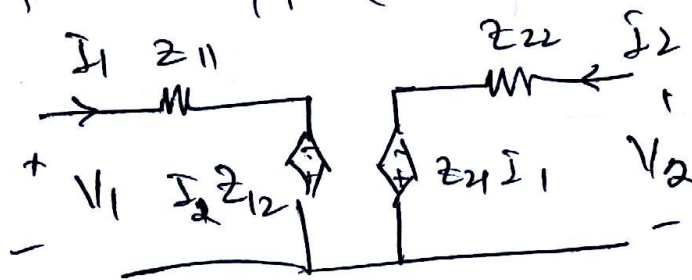

KVL - long method

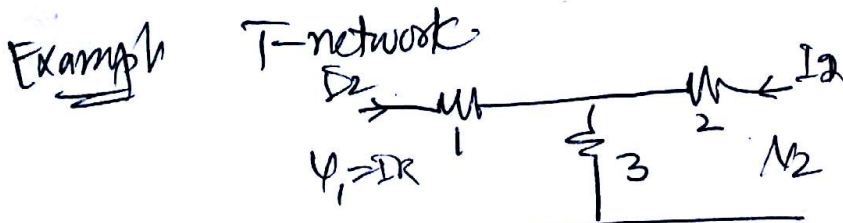

Find Z-parameters

Soln

$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \end{aligned}$$

$$\begin{aligned} V_1 &= 4I_1 + I_2(3) \\ &= 4I_1 + 3I_2 \\ V_2 &= I_1(3) + I_2(2+3) \\ &= 3I_1 + 5I_2 \end{aligned}$$

$$[Z] = \begin{bmatrix} 4 & 3 \\ 3 & 5 \end{bmatrix} \checkmark$$



$$Z_{11} = R_a + R_L$$

$$Z_{22} = R_L + R_c$$

$$Z_{21} = Z_{12} = (T \text{ post-element}) = R_L$$

Method 2

Solving for Y-parameters

$$V_1 = 4I_1 + 3I_2 \quad \text{--- (1)}$$

$$V_2 = 3I_1 + 5I_2 \quad \text{--- (2)}$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \quad \text{--- (3)}$$

put  $V_2=0$  in (2)

$$0 = 3I_1 + 5I_2 \quad \text{--- (3a)}$$

$$I_2 = -\frac{3}{5}I_1 \quad \text{put in (1) --- (1)}$$

$$V_1 = 4I_1 + 3\left(-\frac{3}{5}\right)I_1$$

$$V_1 = 4I_1 - \frac{9}{5}I_1$$

$$V_1 = \frac{20I_1 - 9I_1}{5}$$

$$\frac{V_1}{I_1} = \frac{11}{5}$$

$$\frac{I_1}{V_1} = Y_{11} = \frac{5}{11}$$

$$Y_{12} = \frac{I_1}{V_2}$$

use eqn (1) and (3a)

$$V_2 = 3I_1 + 5\left(-\frac{3}{5}\right)I_1$$

$$\frac{V_2}{I_1} = 3 - 3 = 0$$

$$Y_{12} = \frac{I_1}{V_2} = \infty$$

check?

# Y-parameters

(3)

a)  $V = I Z$  actually.  
 $V = Y^{-1} I$

$$Y^{-1} Y = I$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$I_1 = V_1 Y_{11} + V_2 Y_{12}$$


$$I_2 = V_1 Y_{21} + V_2 Y_{22}$$

put  $V_1 = 0$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} \quad \rightarrow \quad Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

put  $V_2 = 0$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} \quad \rightarrow \quad Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

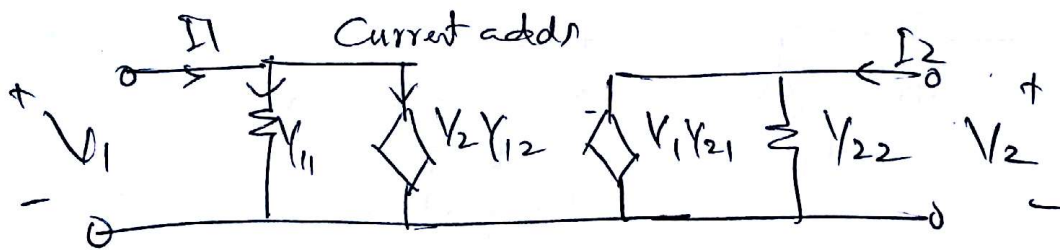

$$Y^{-1} = Z^{-1}$$

~~admittance~~  
 not calc  
 $Y_{11} = \frac{I_1}{V_1}$

H-parameters

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$



$$I_1 = 0$$

$$\frac{V_1}{V_2} = h_{12} \Rightarrow h_{21} = \frac{I_2}{I_1}$$

$$I_2 = 0$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{22} = \frac{I_2}{V_2}$$

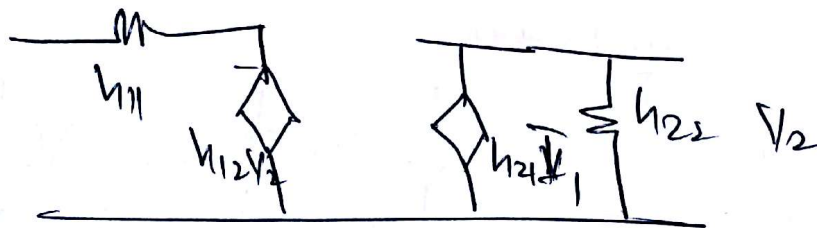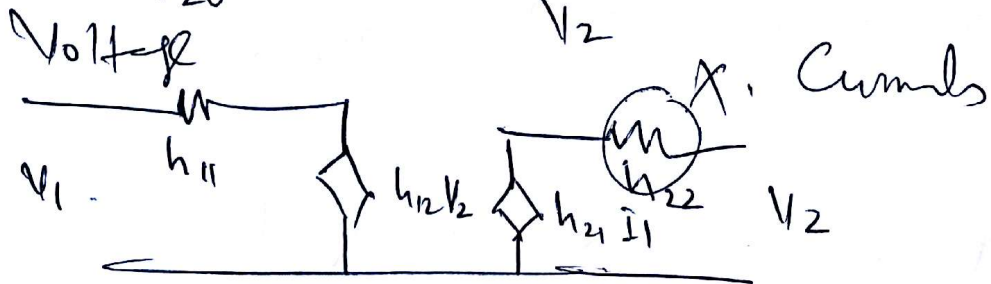

T-parameters

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$




$$B = \left. -\frac{I_1}{I_2} \right|_{V_2=0}$$

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$D = \left. -\frac{I_1}{I_2} \right|_{V_2=0}$$



Cascade conn.

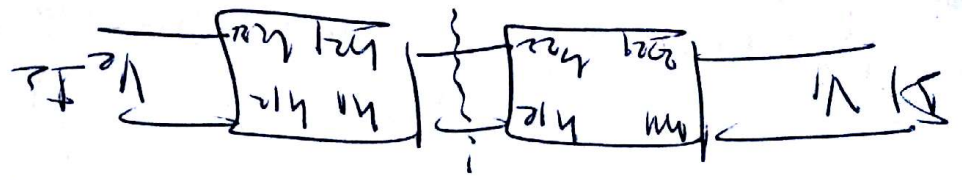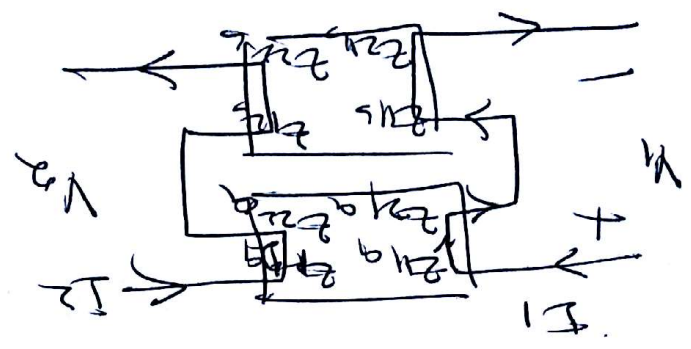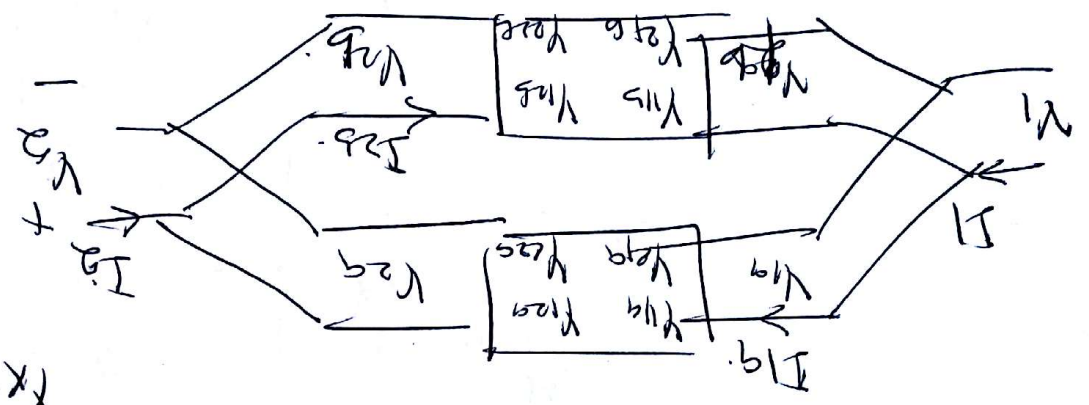

odd  $X_{xy} = X_{xx} + Y_{yy}$


parallel

odd

odd  $Z_{xy} = Z_{xx} + Z_{yy}$


odd  $Y_{xy} = Y_{xx} || Y_{yy}$

Example

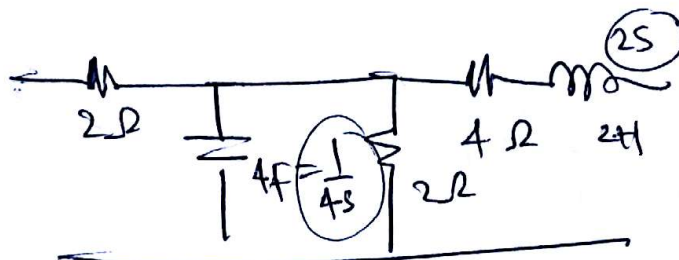

Find  $[Z]$

becomes

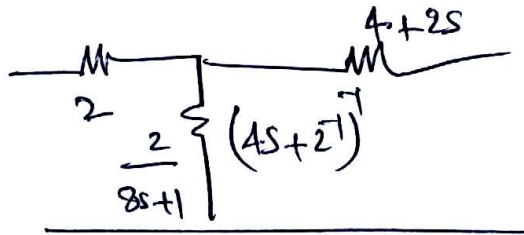

$$Z_{11} = 2 + \frac{2}{8s+1}$$

$$Z_{12} = \frac{2}{8s+1}$$


$$Z_{21} = \frac{2}{8s+1}$$

$$Z_{22} = 4+2s + \frac{2}{8s+1}$$

$$[Z] = \begin{bmatrix} 2 + \frac{2}{8s+1} & \frac{2}{8s+1} \\ \frac{2}{8s+1} & 4+2s + \frac{2}{8s+1} \end{bmatrix}$$

$$[Y] = \frac{1}{[Z]} = [Z]^{-1}$$

Example

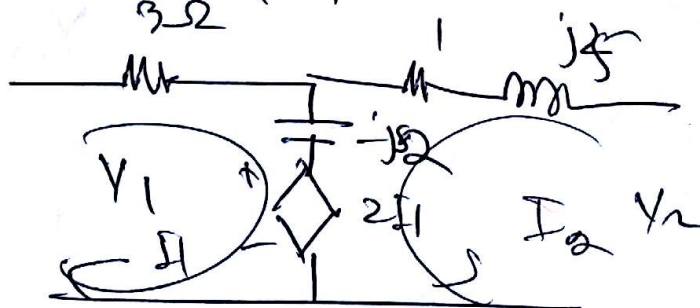

$$V_1 = 3I_1 - j2(I_1 + I_2) + 2I_1$$

$$V_1 = (5-j2)I_1 - (j2)I_2$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$Z_{11} = 5-j2$$

$$Z_{12} = 2j$$


$$Z_{21} = 2j$$

$$Z_{22} = ?$$

solve for second loop

$$V_2 = I_1(-2j) + 2I_1 + I_2(5+1-2j)$$



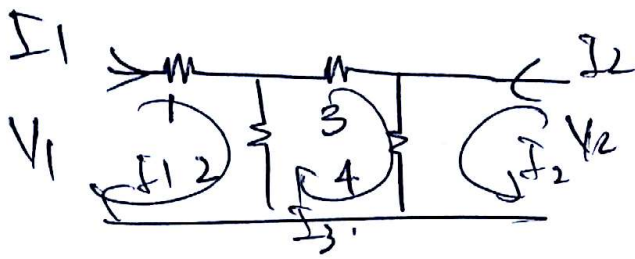

2: loop <sup>(5)</sup>  
 4: Node.

Loop 1

$$V_1 = I_1(1+2) - I_3(2)$$

$$V_1 = 3I_1 - 2I_3 \quad \text{--- (1)}$$

$$0 = -I_1(2) + I_2(4) + I_3(2+3+4)$$

$$0 = -2I_1 + 4I_2 + 9I_3 \quad \text{--- (2)}$$

$$V_2 = 4I_2 + I_3$$

$$4I_2 = \frac{V_2 - 4I_3}{4} \quad \text{--- (3) put in (2)/(1)}$$

$$I_2 = \frac{V_2 - 4I_3}{4} \quad \text{elements } I_2$$

$$I_3 = \frac{V_2 - 4I_2}{4} \quad \text{elements } I_3 \checkmark$$

$$V_1 = 3I_1 - 2\left(\frac{V_2 - 4I_2}{4}\right)$$

$$V_1 = 3I_1 - \frac{2V_2}{4} - \frac{2 \cdot 4I_2}{4}$$

$$V_1 = 3I_1 - \frac{V_2}{2} - 4I_2$$

$$2V_1 = 6I_1 - V_2 - 8I_2$$

$$\boxed{6I_1 + 4I_2 = 2V_1 + V_2} \quad \text{similarly put in --- (3)}$$

for  $I_1 = 0$

$$4I_2 = 2V_1 + V_2$$

for both (1) and (3)  $23I_1 + 0I_2 = 9V_1$   $\text{--- (4)}$

if  $I_2 = 0$

$$\frac{V_1}{I_2} = \frac{2V_2}{9}$$

continue for rest