


(1)

$$\frac{d}{dt}: \quad \lambda = N\phi = L \dot{i}$$

$$\frac{d\lambda}{dt} = N \frac{d\phi}{dt} = L \frac{di}{dt}$$

$$v = \frac{d\lambda}{dt} = N \frac{d\phi}{dt} = L \frac{di}{dt}$$

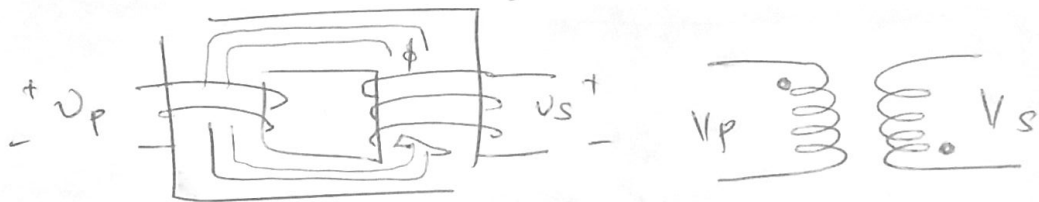Lenz's law gives direction to the produced voltage
 - Voltage is produced by change in ϕ or i
 - ϕ is magnetic change, i is electric change.



$$v_p = \frac{N_1 d\phi}{dt} = L \frac{di_1}{dt}$$

$$v_s = \frac{N_2 d\phi}{dt}$$

no i_2 so no ϕ_2 $N_2 = \text{Coils of 2nd}$

$$N_1 \phi_1 = L_1 i_1 \quad \therefore \quad \phi = \frac{L_1}{N_1} i_1$$

$$\phi_1 = \frac{L_1}{N_1} i_1$$

$$M = \sqrt{L_1 L_2}$$

$$v_s = \frac{N_2 d(L_1 i_1)}{N_1 dt}$$

$M_{21} = \text{Mutual ind in 2 due to 1 (current in 1)}$

$$v_s = \frac{N_2 L_1}{N_1} \frac{di_1}{dt}$$

$$v_s = M_{21} \frac{di_1}{dt}$$


$X_{M_{21}} = j\omega M_{21}$
when fully coupled.

$$|M_{21}| = |M_{12}|$$

M_{ij} can be +ve or negative $j = \text{from}, i = \text{in}$

▷ Dot Notation Rules

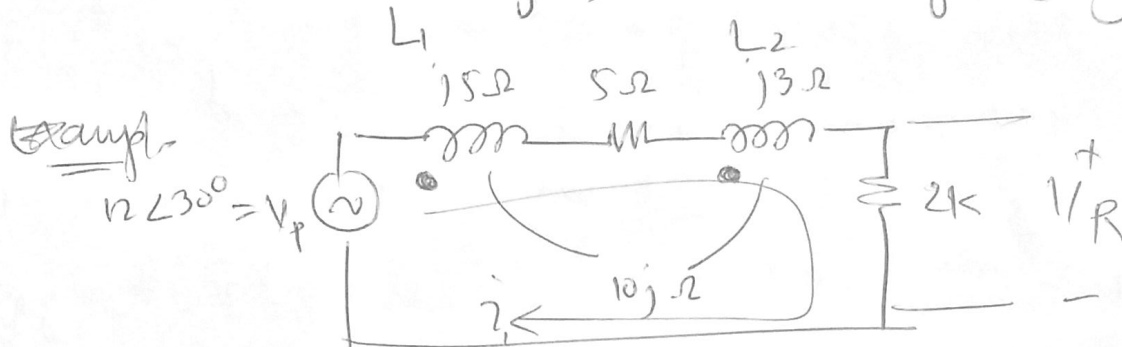- Dot not present \Rightarrow no inductance in mutual
- Leaving current from dot on both coils (+ve)
- Entering " in " " " " " (+ve)
- one leaving \Rightarrow other entering (negative).



Find V_R

using KCL

$$V_{in} = V_{out} + V_{drop}$$

$$V_{in} = V_{out} + V_{separate} + V_{mutual} \text{ (in each)}$$

$$12\angle 30^\circ = i_1(5 + 2k + 5j + 3j) + \underbrace{i_1}_{in L_1}(10j) + \underbrace{i_1}_{in L_2}(10j)$$


$$12\angle 30^\circ = i_1(2005 + j28)$$

$$i_1 = \frac{12\angle 30^\circ}{2005 + j28} = \frac{12\angle 30^\circ}{2005.19\angle 0.8^\circ}$$

$$i_1 = 5.99\angle 29.18^\circ$$

$$V_R = i_1 R = 2k(5.99\angle 29.18^\circ)$$
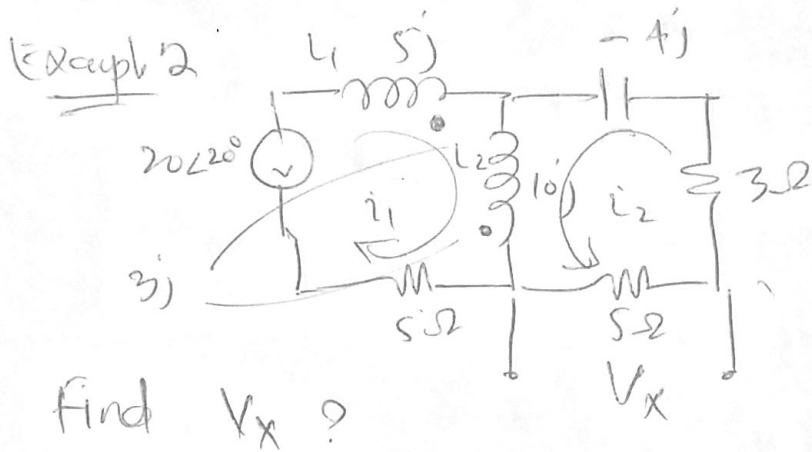
$$V_R = 11.96\angle 29.18^\circ \text{ volts}$$



$$i_1: \quad 20\angle 20^\circ = i_1(5j + 10j + 5) + i_2(10j) \quad (\text{without } L_1, L_2 \text{ in } M)$$

$$20\angle 20^\circ = i_1(15j + 5) + i_2(10j) + \underbrace{i_1(10j)}_{\text{in } L_2 \text{ due to } i_1} + \underbrace{(i_1 + i_2)(10j)}_{\text{in } L_1 \text{ due to } i_1 + i_2}$$

$$20\angle 30^\circ = i_1(5 + 45j) + i_2(20j) \quad \text{--- (1)}$$

$$i_2: \quad 0 = i_1(10j) + i_2(10j - 4j + 3 + 5) \quad (\text{with } M)$$

$$0 = i_1(10j) + i_2(8 + 6j) + \underbrace{i_1(10j)}_{\text{in } L_2 \text{ due to } i_1}$$

$$0 = i_1(20j) + i_2(8 + 6j) \quad \text{--- (2)}$$

$$i_1 = \frac{-i_2(8 + 6j)}{20j}$$

$$20\angle 30^\circ = -\frac{i_2(8 + 6j)}{20j} + i_2(20j)$$

$$400\angle 120^\circ = -i_2(8 + 6j) - 400i_2$$


$$400\angle 120^\circ = -i_2(-392 + 6j)$$

$$i_2 = \frac{-400\angle 120^\circ}{-392 + 6j} = \frac{400\angle 120^\circ}{392.04\angle 179.1^\circ}$$

$$i_2 = 1.0204\angle -59.1^\circ$$

$$V_x = 5(1.02\angle -59.1^\circ) = 5.1\angle -59.1^\circ \text{ volts.}$$

Impedance Conversion;

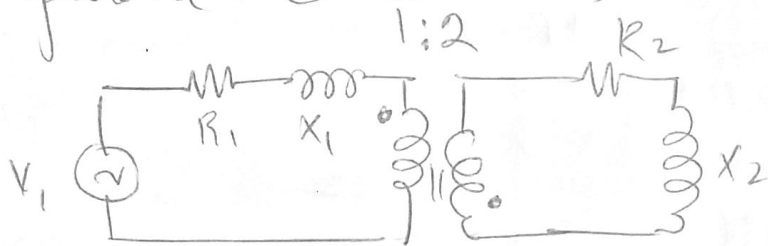

$$P_1 = P_2 \quad // \quad S_1 = S_2$$

$$I_1^2 Z_1 = I_2^2 Z_2$$


$$\frac{I_1}{I_2} = \frac{N_2}{N_1} = \frac{V_2}{V_1}$$

$$\frac{I_1^2}{I_2^2} = \frac{Z_2}{Z_1} = \frac{N_2^2}{N_1^2}$$

$$Z_1 = Z_2 \left(\frac{N_1^2}{N_2^2} \right) = Z_2 \left(\frac{N_1}{N_2} \right)^2 = Z_2 (TR)^2$$

Thus step up transformer makes secondary resistance lesser (visibility will be less) on primary side.

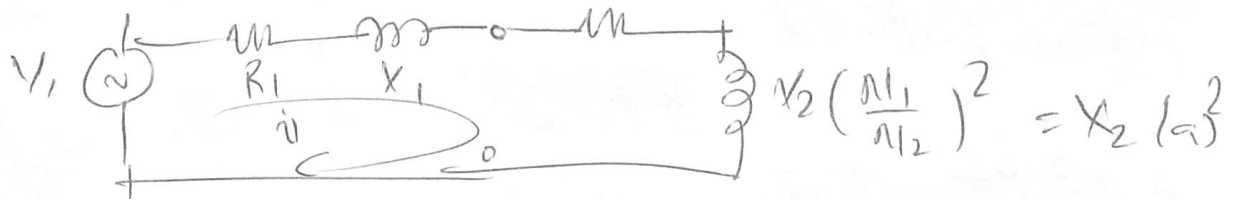Circuit will be as $\left(\frac{N_1}{N_2} \right)^2 \times R_2$




Now you can solve it as single loop equation.

$$V_1 = i (R_1 + X_1 + a^2 R_2 + a^2 X_2)$$

Write KVL equations for following coupled circuit

(3)

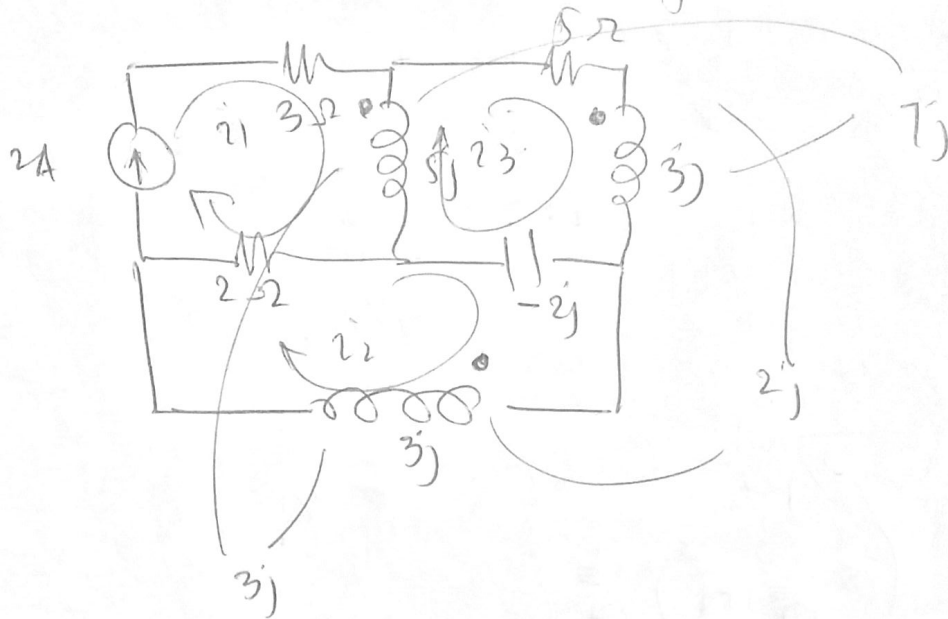

$$i_1 = 2A \quad \text{--- (1)}$$

$$0 = i_1(3 + 5j + 2) - i_2(2) - i_3(5j) + i_2(3j) - i_3(7j)$$

$$i_1: \quad 0 = i_1(5 + 5j) + i_2(3j - 2) + i_3(-12j) \quad \text{--- (2)}$$

$$i_2: \quad 0 = i_2(2 + 3j - 2j) - i_1(2) + i_3(+2j) + (i_1 - i_3)(3j) + i_3(2j)$$

$$0 = i_1(3j - 2) + i_2(2 + j) + i_3(1j) \quad \text{--- (3)}$$

$$i_3: \quad 0 = -i_1(5j) + i_2(+2j) + i_3(5 + 6j) + 7j(i_1 - i_3) + 2j(i_2) - 7j(i_3) + 2j(i_2)$$

$$0 = i_1(-5j + 7j) + i_2(2j + 2j + 2j) + i_3(5 + 6j - 7j - 7j)$$

$$0 = i_1(2j) + i_2(6j) + i_3(5 + 8j) \quad \text{--- (4)}$$