



**Basic Electrical Engineering (EE-154)**  
**Final Term Examination - Spring (2017)**


**Time Allowed: 2hrs**

**Max Marks: 50**

**DIRECTIONS:**

1. Do NOT include unnecessary details and not to exceed 4 lines for a theory question having 2 or less marks.
2. No sharing of calculators or any helping material is allowed during exam.
3. Write your university registration numbers on answer sheets.

**Q: No. 1:** Find the individual and Total Power **S**, Active Power **P** and Reactive Power **Q** for the circuit given by Fig. 1; (10)

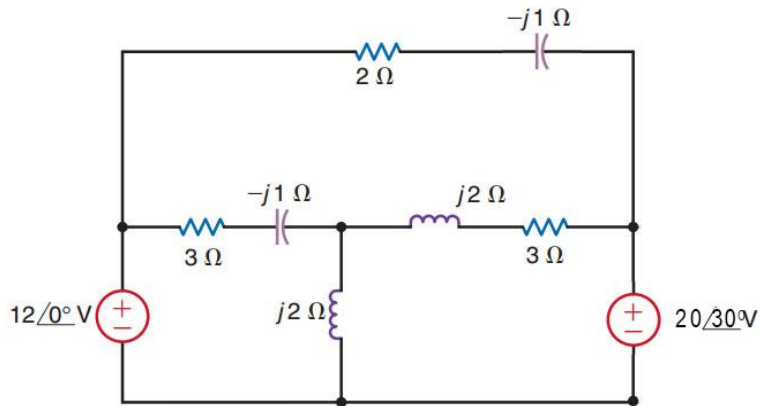

**Fig. 1**

**Q: No. 2:**

- a) What is the significant role of capacitors in eliminating the effect of Inductance in an electrical system? (2)
- b) A series RC circuit consists of **200-Ω** resistive element and a capacitor of **5μF**. For what value of frequency( $f$ ), the circuit will give **300-Ω** impedance? (2)
- c) A parallel RLC circuit has a resistance of **50-Ω**, a Capacitance of **5μF** and an inductor of **20mH**. Find the frequency for which the reactance of capacitor will be equal to the reactance of inductor. (4)
- d) For part (c), find the total circuit current  $i_T(t)$ , when a voltage  $v(t) = 12\sin(2 \times 60 \times \pi + 60^\circ)$ -volts is applied to energize the circuit (2)

**Q: No. 3:**

- a) Find the total heat dissipated by a sinusoidal voltage given by  $v(t) = 1 + 12\sin(100\pi t)$  across a **50Ω** load. (8)
- b) Draw the voltage  $v(t)$  and the current  $i(t)$  on a single graph for part (a). (2)



**Q: No. 4:** Give short answers to the following questions.

(2x5=10)

- If **KVarh** is the unit of an energy meter that is being used to find consumed energy by a system, what type of circuit element(s) will be neglected by such energy meter for energy calculation?
- Why is the rating of a transformer given in **KVA** and not specified in **KW**?
- A certain circuit consists of two points A and B. It is assumed that both the points are at zero potential. The only difference is that, point A quenches all the current/electrons that reaches to it while point B doesn't do so. What is the difference between point A and B?
- What will be the resultant phasor ( $Ie^{j(\omega t + \phi)}$  or  $I \angle \phi$ ) of two instantaneous currents given by;

$$i_1(t) = 12 \sin(\omega t)$$

and

$$i_2(t) = 10 \cos(\omega t)$$

- The turn ratio ( $N_2/N_1$ ) of a certain current transformer (CT) is **200/5**. What will be the value of output current if the CT is mounted on a BUS bar drawing **140A** current at **11KV**?

**Q: No. 5:** A parallel magnetic circuit is given in Fig. 2.

[ $A_e$ : effective Area,  $l_e$ : effective length,  $\mu_r$ : relative permeability]

- Draw the equivalent electrical circuit. (4)
- Find the net reluctance of the circuit given in Fig. 2 and calculate the magnitude of flux between point (a) and point (b) as in given figure if  $MMF = 20 - At$ . (6)

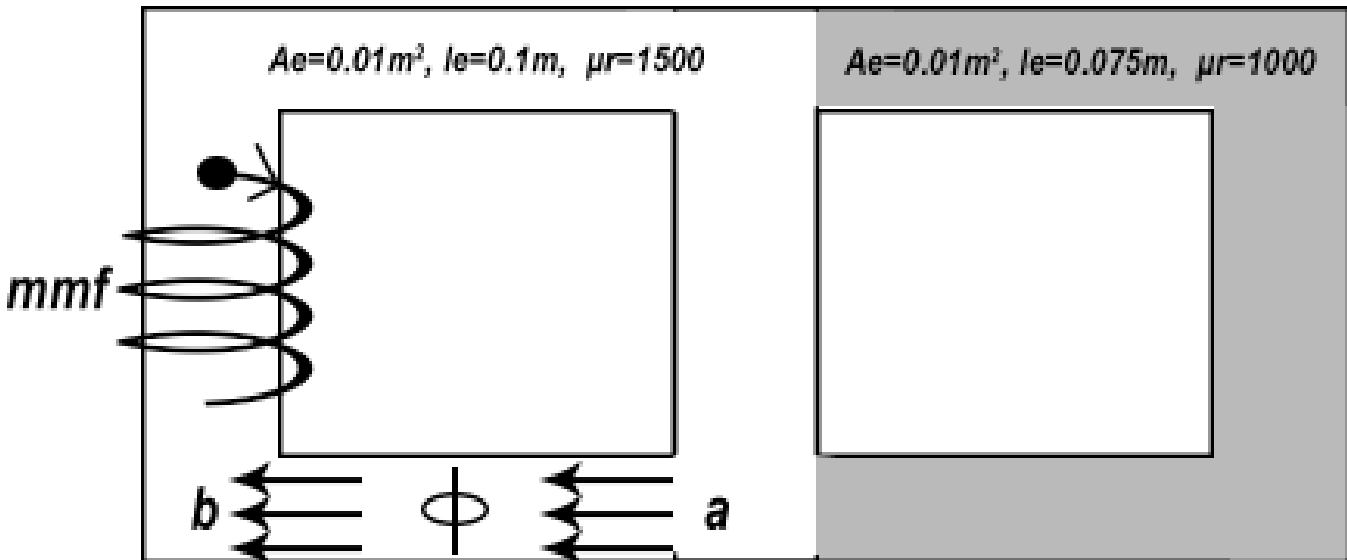


Fig. 2

THE END