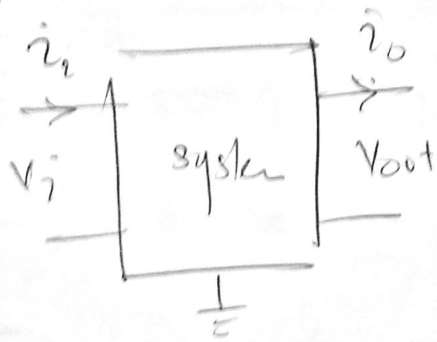


# Transfer function

The characteristics of the system are given by a mathematical function that includes C, L and R. This function is dependent upon frequency.

▷ T/F is also called network function / system function



$$\frac{V_o(s)}{V_i(s)} = G_v(s) \quad \text{Gain}$$

$$\frac{V_o(s)}{I_i(s)} = \overline{Z}(s) \quad \text{Trans adm}$$

$$\frac{I_o(s)}{V_i(s)} = Y(s) \quad \text{Trans imped}$$

$$\frac{I_o(s)}{I_i(s)} = G_i(s) \quad \text{Gain}$$

Response = Transfer function \* input signal

▷ Semi logarithmic scale is used for finding frequency response on a plot

$$\text{dB} = 20 \log \frac{P_2}{P_1} = 20 \log \frac{V_2}{V_1} = 20 \log \left( \frac{I_2}{I_1} \right)$$

$$H(j\omega) = \frac{\text{poles}}{\text{zeros}} * \text{gain}$$

$$= \frac{K_0(a_0s^2 + a_1s + a_2s + \dots)}{b_0s^4 + b_1s^3 + b_2s^2 + \dots}$$

$K_0$  is independent of frequency

simple poles:  $\left( \frac{1}{T} + s \right)$  quadratic pole:  $(1 + 2\zeta sT + (sT)^2)$

zeta  
↓

What is Band Frequency? (Assignment).

Quality Factor

Reciprocal of  $Q$  for  $f$

$$\cos \theta = \frac{R}{Z}$$

$$\frac{1}{\cos \theta} = Q = \frac{Z}{R}$$

$$Q = \frac{\text{Energy stored}}{\text{Energy dissipated}}$$

$$Q_L = \frac{R + j\omega L}{R} = \left| \frac{j\omega L}{R} \right| \quad R \ll \omega L$$

$$Q = \frac{\omega L}{R}$$

$$Q_C = \left| \frac{R + 1/j\omega C}{R} \right| = \frac{1}{\omega C R} \quad R \ll \omega C$$

$$Q_L = Q_C$$

$$Q^2 = Q_L Q_C = \frac{\omega L}{\omega C R \cdot R} = \frac{L}{R^2 C}$$

$$Q = \sqrt{\frac{L}{R^2 C}} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Also

$$Q = \frac{f_{\text{central}}}{f_2 - f_1} = \frac{f_c}{\Delta f} = \frac{f_c}{\text{Bandwidth}}$$

# Series Resonance Circuit

## Resonance frequency

when  $|X_L| = |X_C|$




$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$


$$\omega_c = \sqrt{\frac{1}{LC}} = \frac{1}{\sqrt{LC}}$$

$$2\pi f_c = \frac{1}{\sqrt{LC}}$$


$$f_c = \frac{1}{2\pi\sqrt{LC}}$$

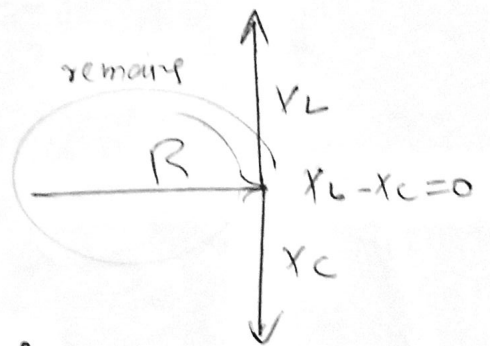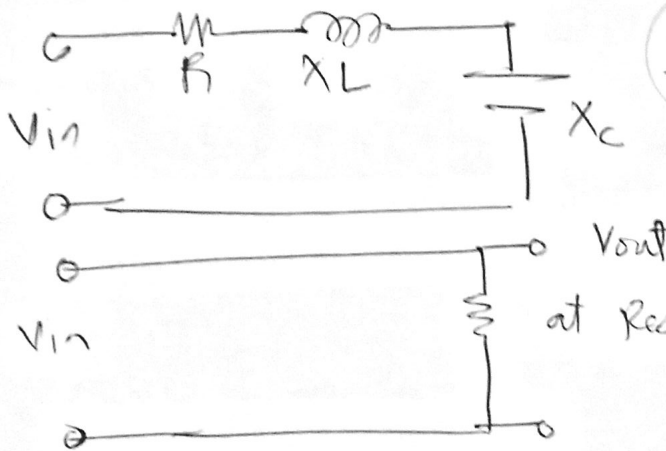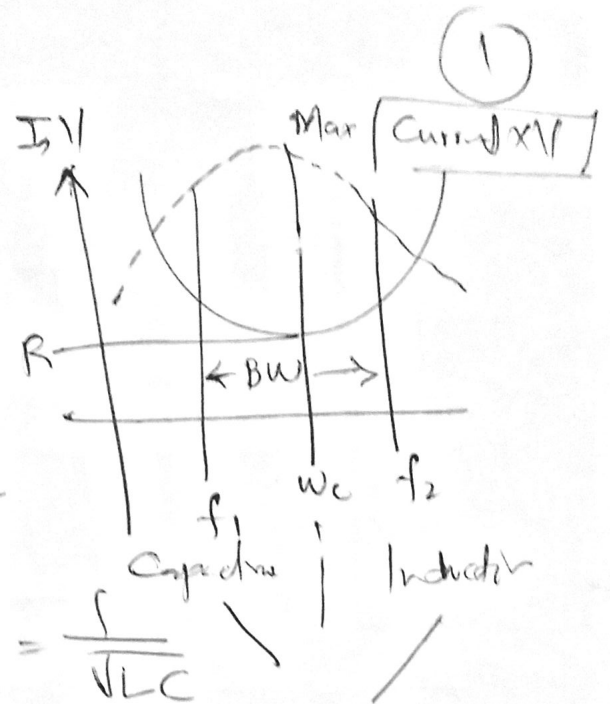


$\omega$	$X_L(\omega L)$	$X_C(\frac{1}{\omega C})$	$R$	$Z$	$V$	$I$
0	0	$\infty$	$R$	$\infty$	-	0
1	$L$	$\frac{1}{C}$	$R$	$R + jL + \frac{1}{C}$	$\frac{V_1}{I_1}$	$I_1 = \frac{V_{in}}{R + jL + \frac{1}{C}}$
10	$10L$	$\frac{1}{10C}$	$R$	$10L + R + \frac{1}{10C}$	$\frac{V_{10}}{I_{10}}$	$I_{10} = \frac{V_{in}}{R + Z_{CL}}$
$\infty$	$\infty$	$\frac{1}{\infty} = 0$	$R$	$\infty$	-	0
$\rightarrow \omega_c$	$j\omega_c L$	$-j\frac{1}{\omega_c C}$	$R$	$R$	$\frac{V}{I}$	$I_{max} = \frac{V_{in}}{R}$

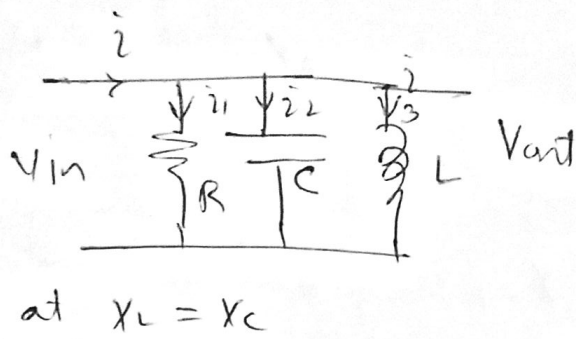

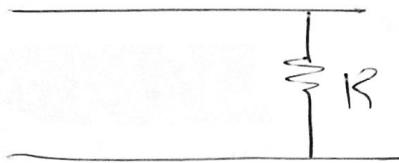2  
 $i$  has multiple paths to flow  
 for  $Z$  is low



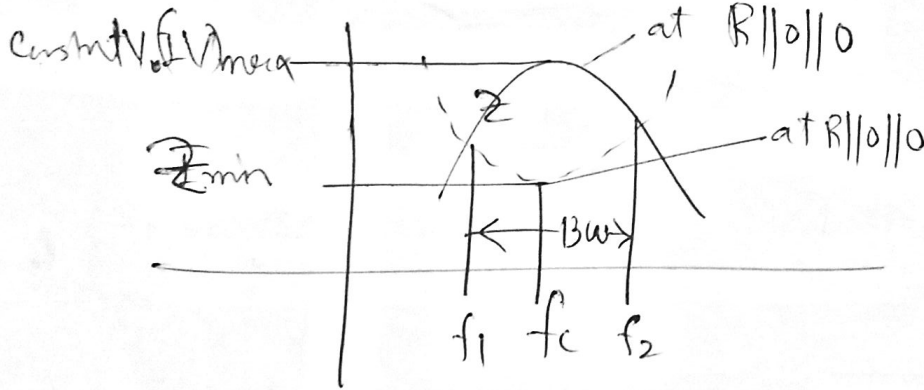$i$  has only one path for its flow  
 $Z = R$  is high  
 BW: Bandwidth



no parallel path results - high  $Z$

Series (reference  $I$ )

at  $\omega_c$

$$X_C = X_L$$

$$Z = R = \text{minimum}$$

Current is in phase with voltage to power transfer is maximum

$\omega < \omega_c$

Voltage lags current

$\omega > \omega_c$

Voltage leads current

Parallel (reference  $V$ )

at  $\omega_c$

$$X_C = X_L$$

$$Z = R = \text{maximum}$$

$P = I V$   $I$  in phase with  $V$   
 So max power transfer

$\omega < \omega_c$

$I$  lags  $V$

$\omega > \omega_c$

$I$  leads  $V$ .